
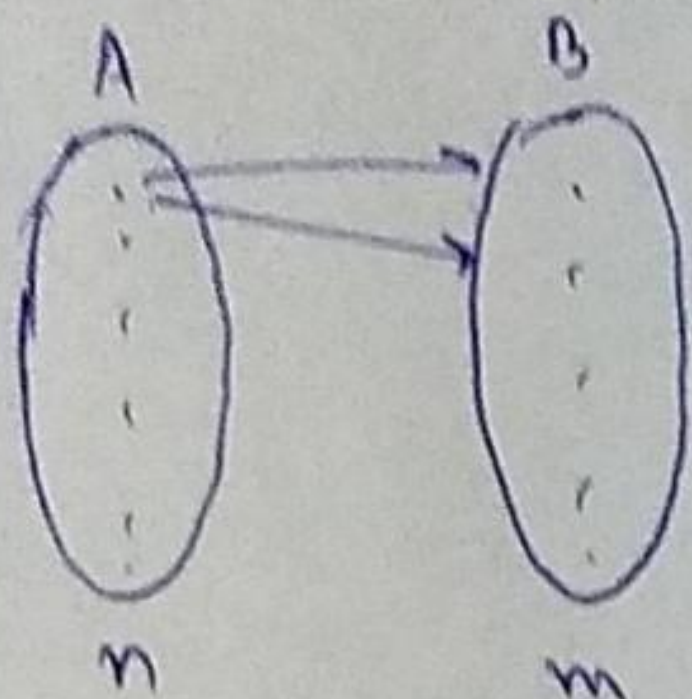


NUMBER OF FUNCTIONS

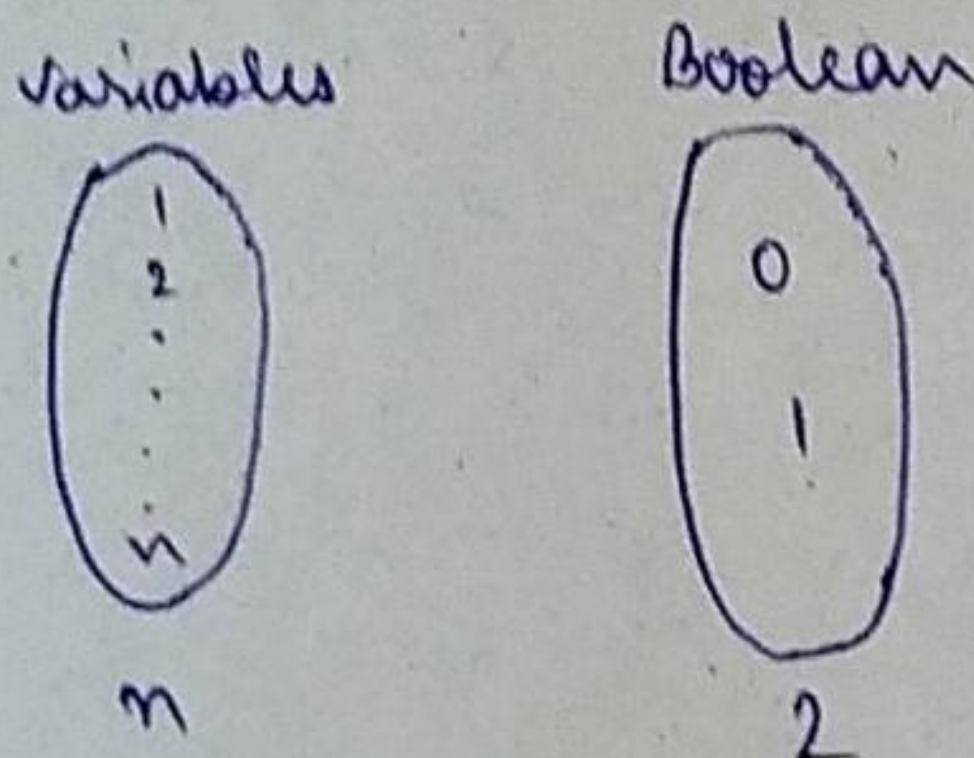

~~For~~ # function = m^n


⊛ For n boolean variables, how many boolean functions?



function = 2^n

function

boolean function

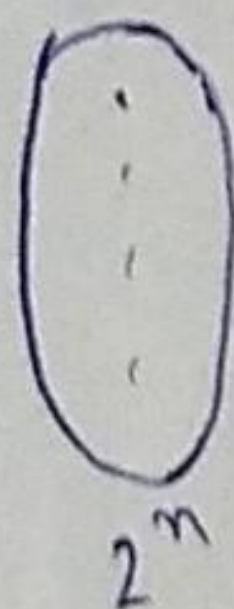

boolean function = 2^{2^n}



So, for n boolean variables,

boolean functions = 2^{2^n}


⊛ For n k -ary variables, how many m -ary functions possible?

[n/k -ary \rightarrow boolean / binary / quaternary / ...]


Variable

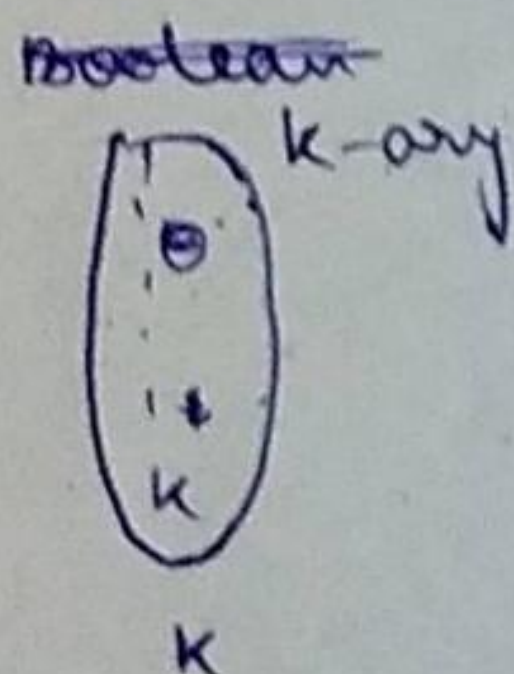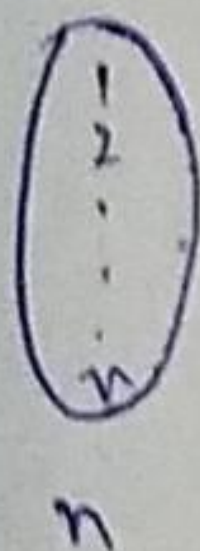

function

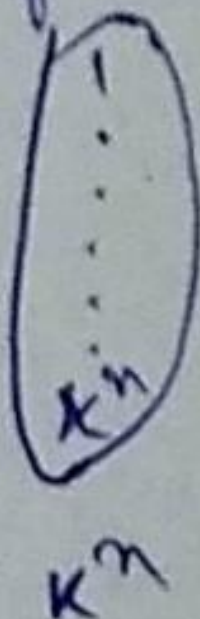

m -ary

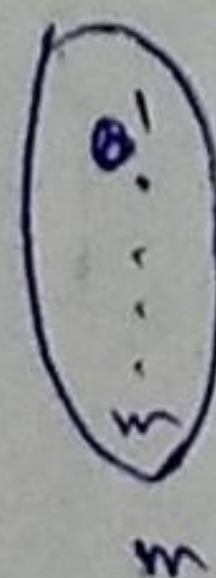

function = k^n

m -ary functions = m^{k^n}

So, for n k -ary variables, number of m -ary

function possible are = m^{k^n}

COUNTING NUMBER OF FUNCTIONS & NEUTRAL FUNCTIONS :

① How many boolean functions are possible with 3 variables such that there are exactly 3 minterms.

→ Total functions for 3 variables (boolean) = $2^3 = 8$.

Value of minterms = 1

For exactly 3 minterms we get 3 ones out of 8 total boolean functions.

a	b	c	
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\text{So, \# of functions} = {}^8C_3 = 56$$

② For at most 3 minterms,

$$\text{\# of functions} = {}^8C_0 + {}^8C_1 + {}^8C_2 + {}^8C_3$$

$$= 1 + 8 + 28 + 56 = 93$$

③ For ' k '-^{boolean} variable and exactly ' m ' minterms

$$\text{\# of function} = {}^{2^k}C_m$$



→ NEUTRAL FUNCTION: A neutral function is a function in which # minterms is equal to # maxterm.

→ For n variables, i.e., 2^n input, and


$$\text{\# minterm} = \text{\# maxterm} = \frac{2^n}{2} = 2^{n-1}$$

$$\text{Then no. of neutral function} = {}^{2^n}C_{2^{n-1}} \quad (\text{for } n \text{ boolean variables})$$


VENN DIAGRAM REPRESENTATION

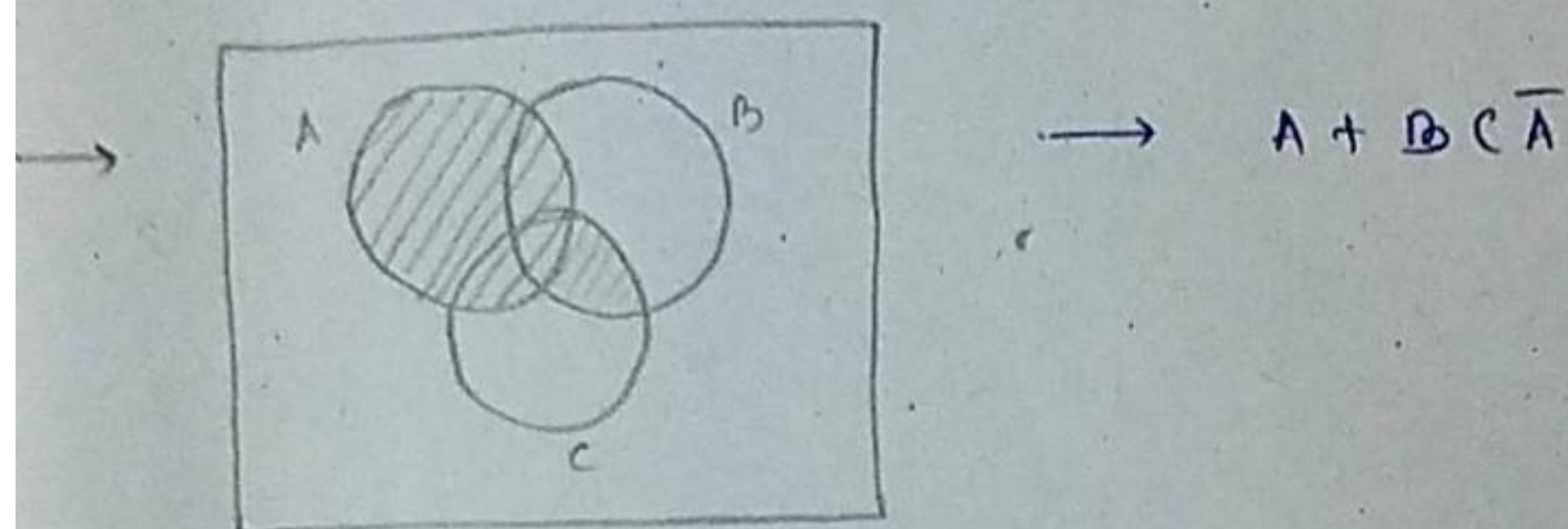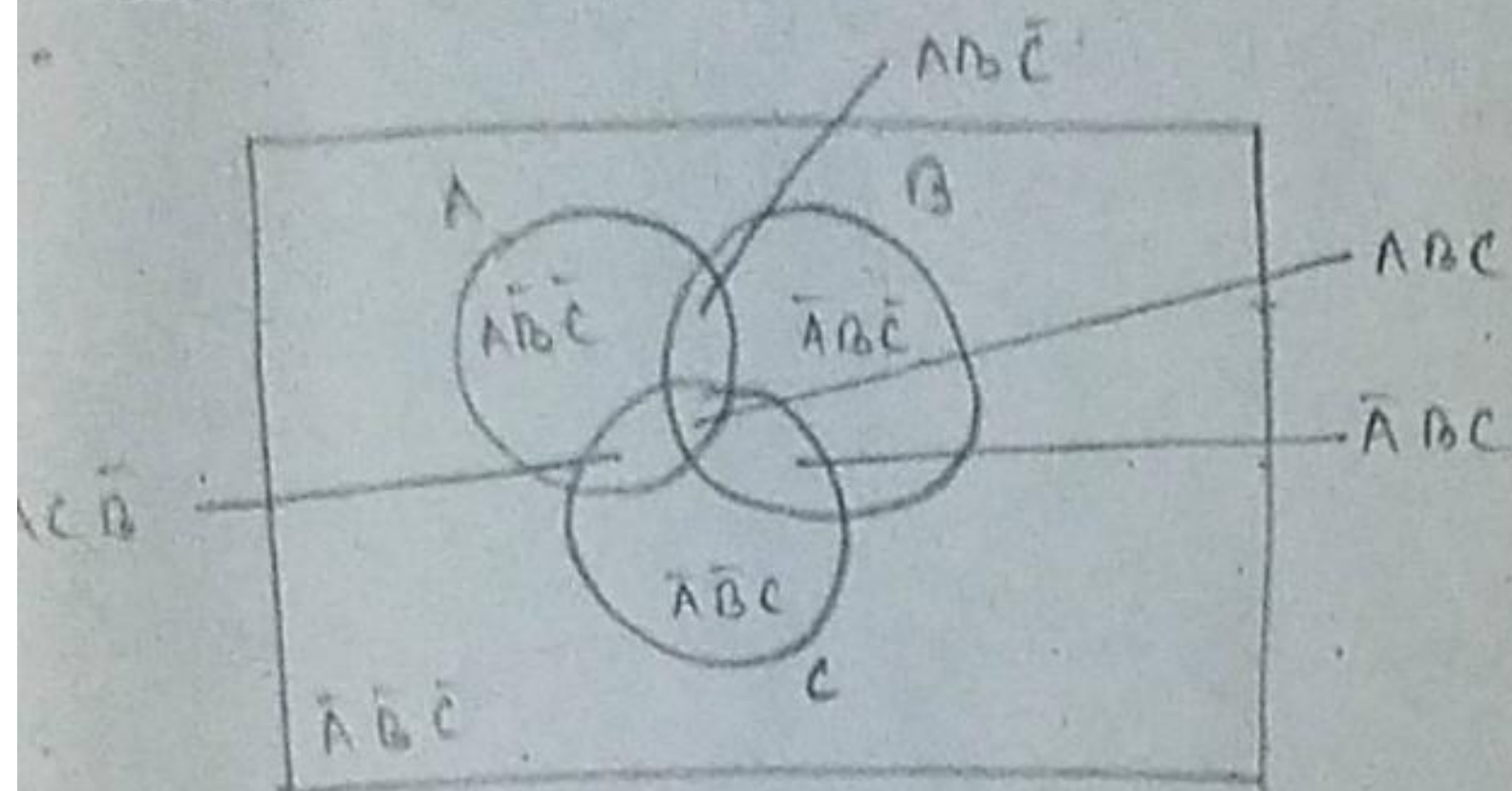

of possible shadings = $2^{2^3} = 256$

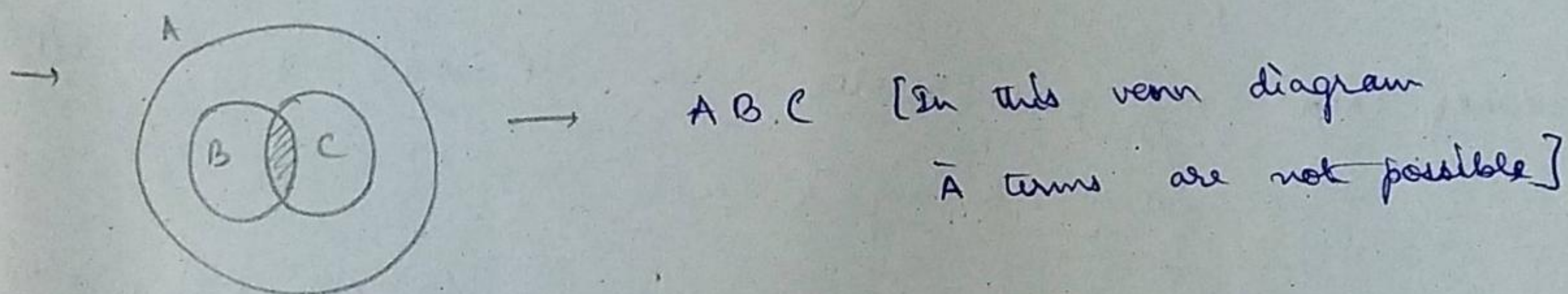

CONTACT REPRESENTATION :-

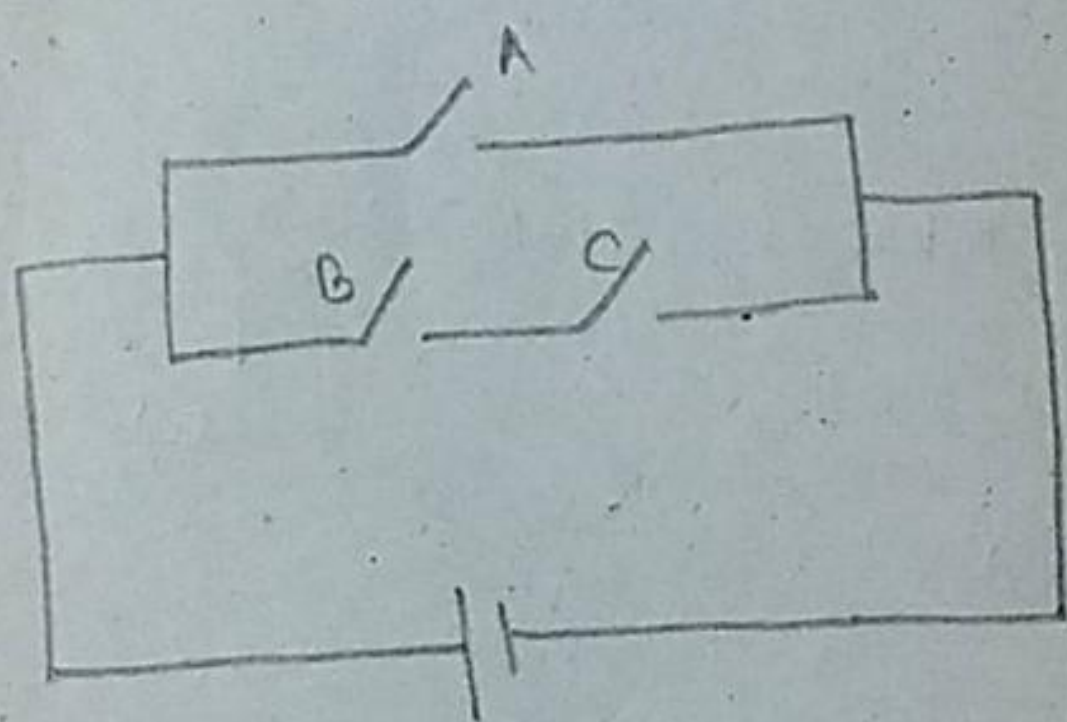

→ Every boolean function can be represented with the help of serial and parallel contact.

→ B and C (Serial contact)

A and C (Parallel contact)


→ Serial contacts are performing 'AND' operation.

"OR" "

→ Parallel contacts ~ ~ ~


→ The given circuit will pass current if either A is closed

or both B and C are closed i.e. $A + BC$

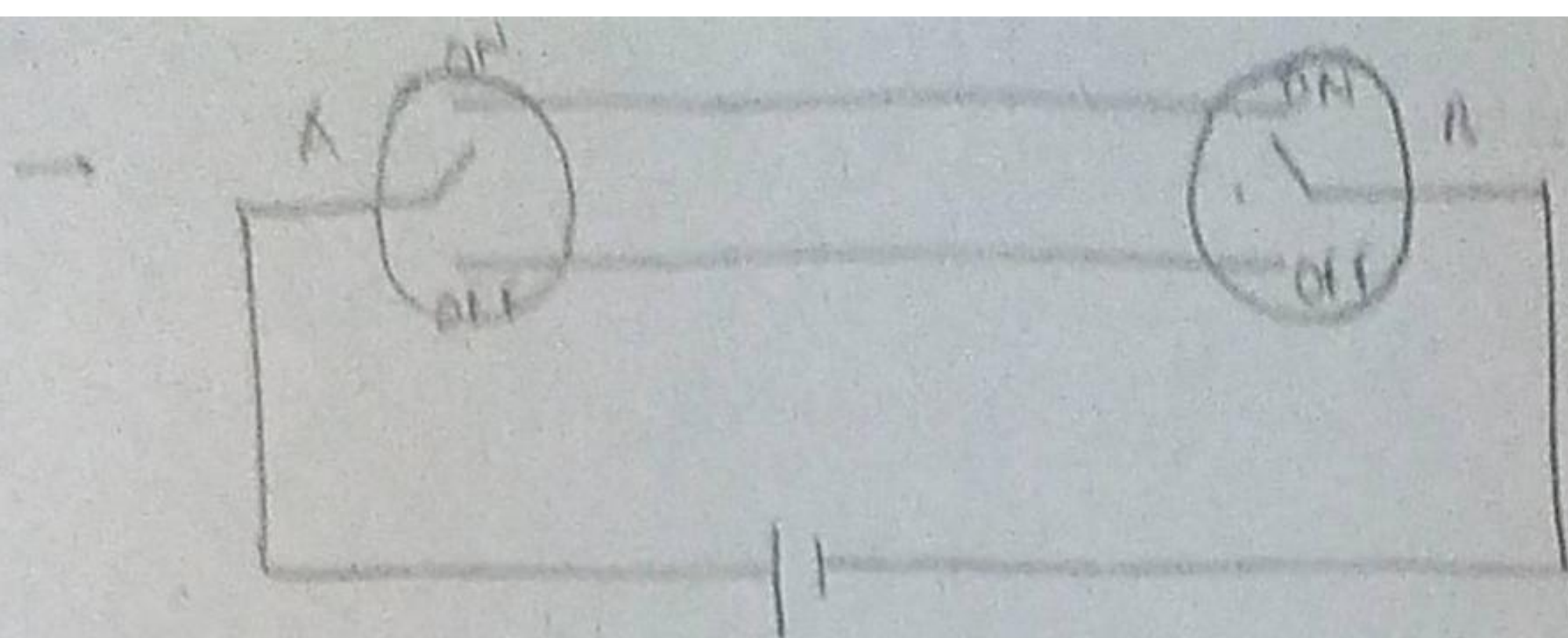

$$\rightarrow AB + \overline{A}\overline{B} \rightarrow \text{XNOR}$$

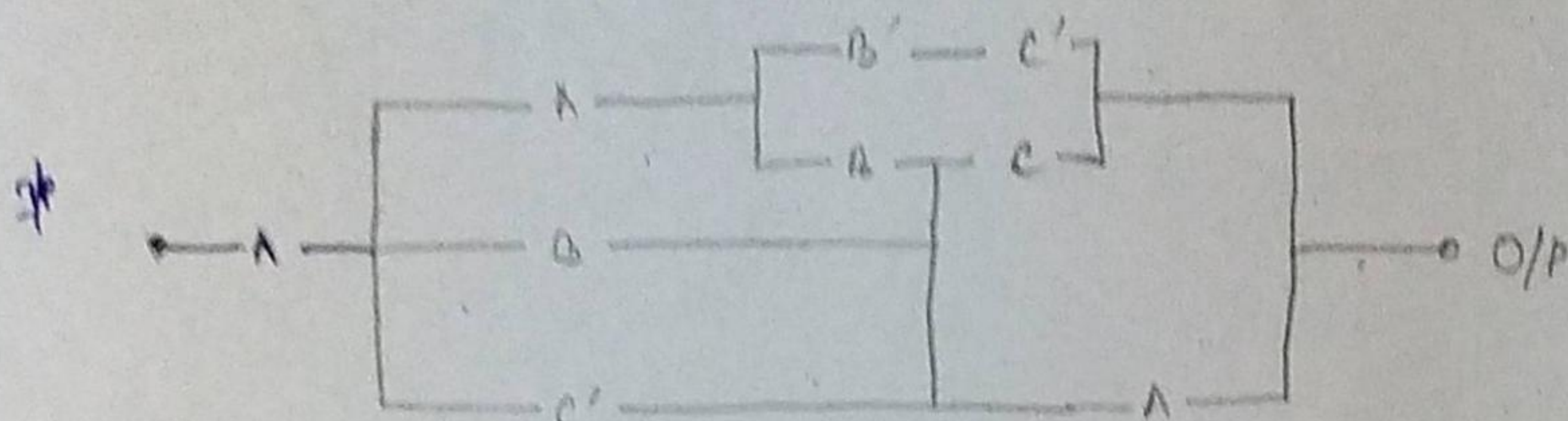→ Identify the boolean expression given by following circuit.



- Find the valid forward path
- Perform OR among them

FORWARD PATH : Any path starting from I/P and ending at O/P without forming a cycle.

VALIDITY : No path should contain a variable in both true and complemented form.

$$b) \rightarrow A\overline{A}\overline{B}\overline{C} + A\overline{A}BC + A\overline{A}BA + ABC + ABA + \underbrace{A\overline{C}\overline{C} + A\overline{C}A}_{\text{Invalid}}$$

= Simplify it and get result.

NESTED FUNCTION :-

→ In the following simultaneous boolean expressions, what are the values of w, x, y, z .

$$x + y + z = 1$$

$$xy + \bar{w}\bar{z} = 0$$

$$x\bar{w} + y\bar{z} = 1$$

	w	x	y	z
(a)	0	0	0	1
(b)	1	1	0	1
(c)	0	1	0	1
(d)	1	0	0	0

← OPTIONS.

In this type of question we need to check each of the values in the MCQ with the simultaneous equations given in the question and find the correct option.

→ If $f(A, B) = \bar{A} + B$ then find $f(f(x+y, y), z)$

↳ This is called nested function.

$$f(f(x+y, y), z)$$

$$= f(\overline{x+y} + y, z) = f(\bar{x}\bar{y} + y, z)$$

$$= f((\bar{x}+y)(\bar{y}+y), z) = f(\bar{x}+y, z)$$

$$= f(\overline{\bar{x}+y}) + z = \boxed{\bar{x}\bar{y} + z} \quad (\text{Ans.})$$

NAND GATE & PROPERTIES

' \uparrow ' \rightarrow This is symbol for NAND

A	B	$A \uparrow B$
0	0	1
0	1	1
1	0	1
1	1	0

Properties :-

a) Identity : $A \uparrow A = \bar{A}$

A	$A \uparrow A$
0	1
1	0

$$A \uparrow A = \bar{A}$$

So it is not following identity.

b) Commutative :

$$A \uparrow B = \overline{A \cdot B} = \overline{B \cdot A} \quad \{ \text{since AND is commutative} \}$$
$$= B \uparrow A$$

$\therefore A \uparrow B = B \uparrow A$, NAND is commutative.

c) Associativity :

$$A \uparrow (B \uparrow C) = (A \uparrow B) \uparrow C \quad \{ ? \}$$

For, $A = 0$, L.H.S = 1, R.H.S = \bar{C}

So, NAND is not associative.

NOR GATE & PROPERTIES

A	B	$A \downarrow B$	$\overline{A+B}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Properties :-

a) Idempotency : Idempotency is when $A \odot A = A$
 \downarrow
 any operator

$$A \downarrow A = \overline{(A+A)} = \bar{A}$$

So, nor is not idempotent.

b) Commutative : $A \downarrow B = B \downarrow A$

$$A \downarrow B = \overline{A+B} = \overline{B+A} = B \downarrow A$$

So, nor is commutative.

c) Associative : $A \downarrow (B \downarrow C) = (A \downarrow B) \downarrow C$

For $A=0$

$$1 \odot A \downarrow (B \downarrow C) = 1 \odot \downarrow \overline{(B+C)} = 0 \odot \downarrow \overline{(B+C)} \quad (\text{L.H.S.})$$

$$\text{R.H.S.} = (1 \downarrow B) \downarrow C = \overline{1+B} \downarrow C = 0 \downarrow C = \bar{C} \odot$$

So, NOR is not associative.

EX - OR GATE & PROPERTIES

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

[\because If ~~both~~ associativity holds true for both 0 and 1 substitution, we need to check all values in truth table]

Properties :-

- a) Not Idempotent
- b) Commutative
- c) Associative

NOTE : $\overline{B \oplus C} = \bar{B} \oplus C = B \oplus \bar{C}$

EX - NOR Gate & Properties

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

Properties :-

- a) Not Idempotent
- b) Commutative
- c) Associative

NOTE : $\overline{A \odot B} = \bar{A} \odot B = A \odot \bar{B}$

1) $A \odot B = \bar{A} \oplus B = A \oplus \bar{B}$

2) $A \oplus B = \bar{A} \odot B = A \odot \bar{B}$

PROPERTIES OF EX-OR & EX-NOR

$A \oplus B = 1$ whenever a) number of 1's is odd

b) $\text{sum} \% 2$ is 1

$\odot = 1$ when a) a number of 0's is even

If n is even:

If #1's is odd \Rightarrow #0's is also odd

If #1's is even \Rightarrow #0's is also even

So, \oplus and \odot act as complement for even n.

When n is odd \oplus and \odot are equal to each other.

$A \oplus B$

A \ B	0	1
0	0	1
1	1	0

$A \odot B$

A \ B	0	1
0	1	0
1	0	1

$A \oplus B \oplus C$

A \ B \ C	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$A \odot B \odot C$


A \ B \ C	00	01	11	10
0	1	0	1	0
1	0	1	0	1

EXOR \rightarrow # minterm == # maxterm and 1's where #1's is odd

EX NOR \rightarrow # minterm == # maxterm and 1's where #0's is even


MINIMUM NUMBER OF GATES FOR EX OR & EX NOR

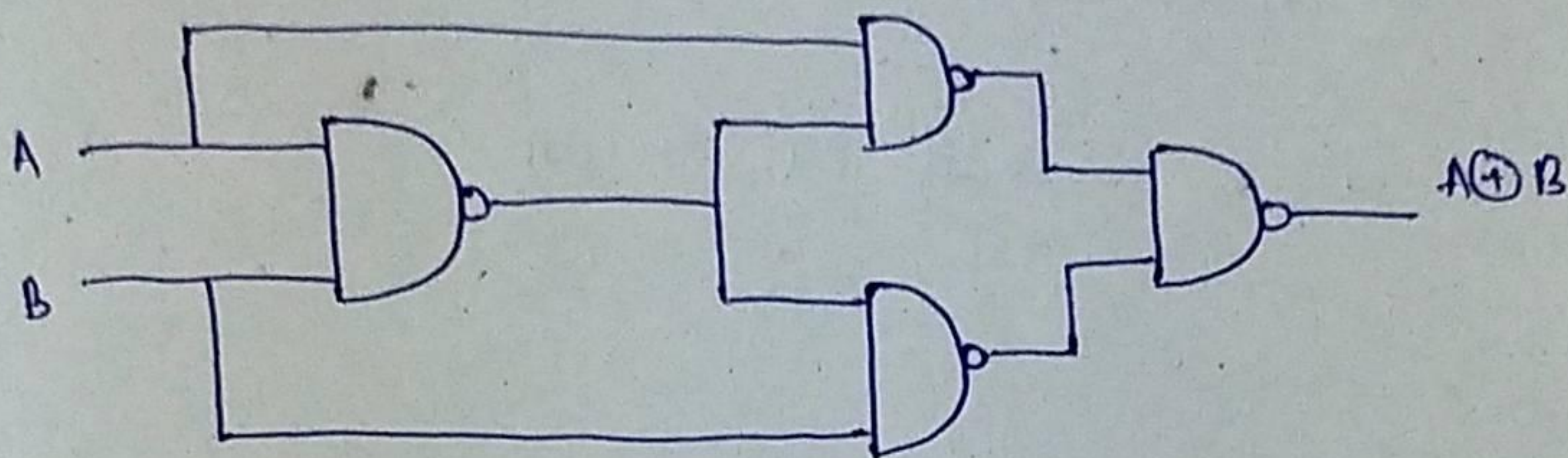① How many NAND gates are required for EX OR?



So, Number of NAND gates required is 4.

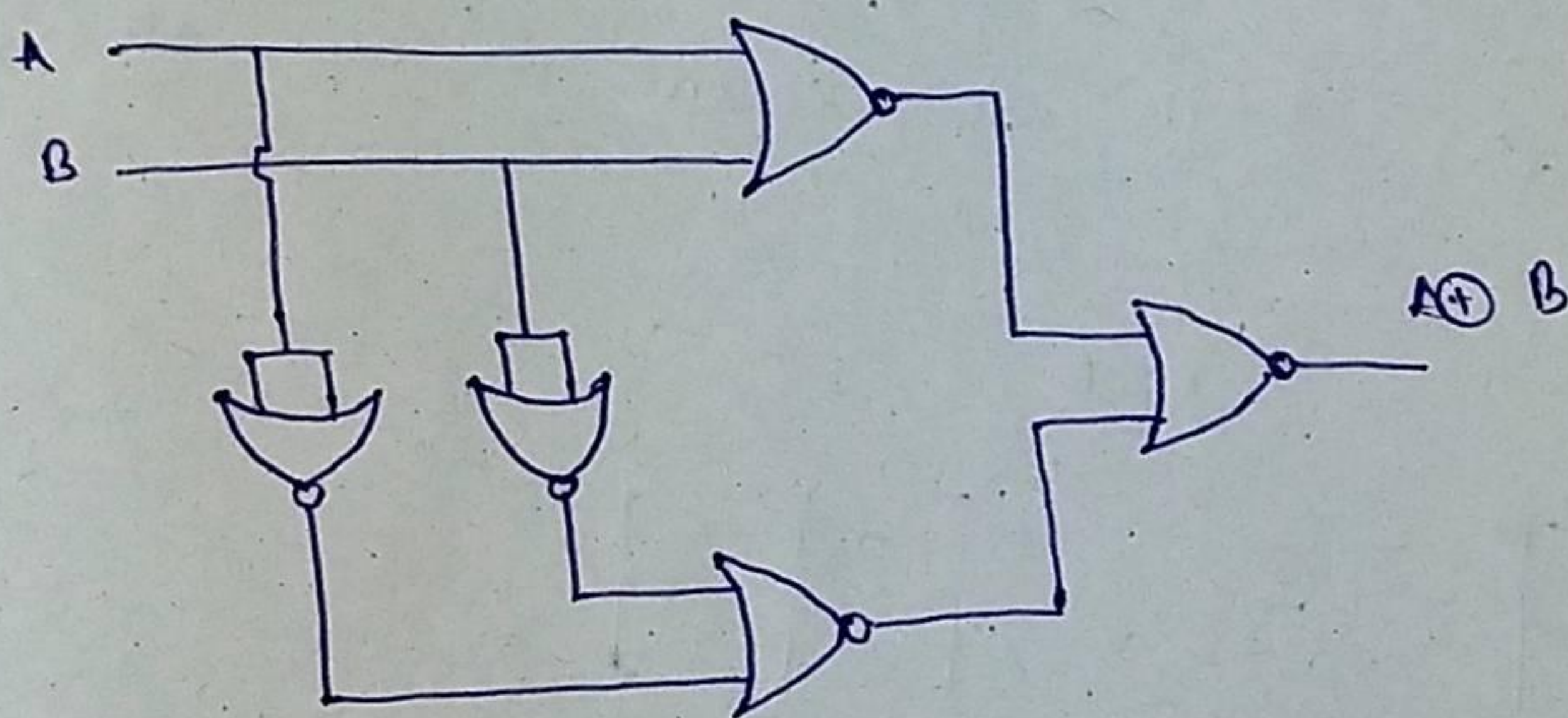② How many NOR gate are required for EX OR? → 5



③ # of NAND gate for EX NOR → ~~4~~ 5

④ # of NOR gate for EX NOR → ~~5~~ 4

FUNCTIONALLY COMPLETE OPERATIONS

A set of operations is said to be functionally complete (or) universal if and only if every switching function can be expressed by means of operations in it.

→ The set $\{+, \cdot, -\}$ is clearly function complete
(complement)

→ The set $\{+, -\}$ is said to be functionally complete

→ The set $\{\cdot, -\}$ " " " " " " " " " " " "

NOTE: A set is functionally complete if we can derive a set which is already functionally complete.

EXAMPLES

$$\textcircled{1} f(A, B, C) = \bar{A} + B\bar{C}$$

$$f(A, A, A) = \bar{A} + A\bar{A} = \bar{A} \rightarrow \text{complement is derived}$$

$$f(f(A, A, A), B, f(B, B, B)) = (\bar{A}) + B\bar{B} = A + B \cdot B = A + B$$

↳ OR is implemented

So, $\{+, -\}$ is getting derived.

$$\textcircled{2} f(A, B) = \bar{A} + B$$

$$f(A, A) = \bar{A} + A = 1, \quad f(B, B) = 1$$

$$f(A, 0) = \bar{A} \rightarrow \text{complement implementation}$$

$$f(f(A, 0), B) = (\bar{A}) + B = A + B \rightarrow \text{OR implemented}$$

$\{+, -\}$ is getting derived

Whenever a function is taking support from 0 or 1, then it is called partially functionally complete.

$$\textcircled{3} \quad f(A, B) = \bar{A}B$$

$$f(A, A) = \bar{A}A = 0, \quad f(B, B) = 0.$$

$$f(\bar{A}, 1) = \bar{A} \rightarrow \text{Complement done.}$$

$$f(f(\bar{A}, 1), B) = \bar{A}B \rightarrow \text{And done.}$$

$(\cdot, -)$ is ~~not~~ derived.

The $f(A, B)$ is partially functionally complete with help of 1

$$\textcircled{4} \quad f(A, B, C) = AB + BC + CA$$

In given expression if there is no complement then it is not ~~not~~ functionally complete.

$$\textcircled{5} \quad f(x, y) = \bar{x}y + x\bar{y}$$

$$f(x, 1) = \bar{x} \cdot 1 + x \cdot 0 = \bar{x} \rightarrow (-) \text{ DONE}$$

$(+)$ or (\cdot) is not implemented

So, f is not FC.

$\textcircled{6}$ Any boolean function can be defined with which of following operations.

a) $\textcircled{1}$, NOT X

b) $\textcircled{+}$, 1, OR \checkmark

c) $\textcircled{+}$, 1, NOT X

d) $\textcircled{\odot}$, 1, NOT

SELF DUAL FUNCTIONS

→ whenever a function is equal to its dual then it is called self dual.

$$f(A, B, C) = AB + BC + CA$$

$$f_d(A, B, C) = (A+B)(B+C)(C+A) = AB + BC + CA$$

→ A boolean function is dual if:-

a) It is neutral (no. of minterms = no. of maxterms)

b) The function does not contain two mutually exclusive terms.

Mutually Exclusive pairs → (0, 7), (1, 6), (2, 5), (3, 4)

$$f = 2 \times 2 \times 2 \times 2 = 16$$

$$\text{No. of pairs} = 2^{n-1}$$

→ ① $f(A, B, C) = \sum(0, 2, 3)$ ✗

This function don't contain mutually exclusive value but

it is not neutral.

② $f(A, B, C) = \sum(0, 1, 6, 7)$ ✗ → contain mutually exclusive

③ $f(A, B, C) = \sum(0, 1, 2, 4)$ ✓ → Neutral + Non mutually exclusive

④ $f(A, B, C) = \sum(3, 5, 6, 7)$ ✓ → ~

INTRO TO ELECTRONIC GATES

- 1) Electronic gates generally receive voltage as input and produce voltage as output.
- 2) The precise value of voltages ~~is~~ are not significant towards determination of logical operation of gates.
- 3) The significant point ~~is~~ that voltages are restricted b/w two limits.
- 4) Two valued variables may be used to represent these voltages.
- 5) If we associate constant '1' with high voltage and '0' with low voltage, it is called (+)ve logic system and for vice versa it is called (-)ve logic system.

⊛ POSITIVE & NEGATIVE LOGIC SYSTEMS ARE DUALS OF EACH OTHER